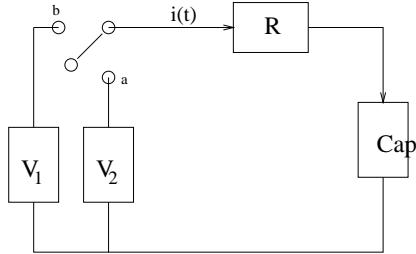


Due: see Organizational Info


**Problem [1].** Consider the circuit shown in the figure with  $R = 1\Omega$  and  $\text{Cap} = 1F$ . The switch is supposed to have been at position a for a long time (say, since  $t = -\infty$ ). At  $t = 0$ , it goes to position b. Find the current  $i(t)$ ,  $t \geq 0$ , for the following values of the two batteries:



- (i)  $V_1 = 0V$ ,  $V_2 = 1V$ ; (ii)  $V_1 = 1V$ ,  $V_2 = 0V$ ; (iii)  $V_1 = 1V$ ,  $V_2 = 1V$ .


Using your answers for (i), (ii), (iii), argue that the current  $i(t)$  can be considered as a sum of the circuit's zero-state response and zero-input response. ■

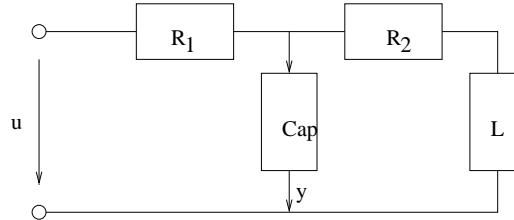**Problem [2].** Consider the RLC circuit shown in the figure. The notation is as follows:  $u$  is the input voltage,  $y$  the output current,  $x_1$  is the voltage across the capacitor and  $x_2$  the current through the inductor. (a) Write state and output equations and determine  $n, m, p$  and  $A, B, C, D$ . Write the i/o



equation of this system in the form  $q(\frac{d}{dt})y = p(\frac{d}{dt})u$  (determine  $q(s)$  and  $p(s)$ ). (b) Assume zero initial conditions and unit value for all elements. Compute the state  $x$ , the transfer function and the impulse response. Hence compute the step response. ■

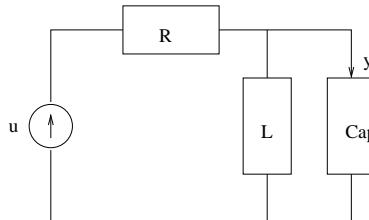**Problem [3].** Given is the RLC circuit shown below.



The input is the current  $u$  provided to the circuit, while the output is the current  $y$  through the capacitor Cap.

(a) Write these equations in the form  $\dot{x} = \hat{A}x + \hat{B}u$ ,  $y = \hat{C}x + \hat{D}u$ , where  $x_1$  is the current through the inductor and  $x_2$  is the voltage across the capacitor; what are the matrices  $\hat{A}$ ,  $\hat{B}$ ,  $\hat{C}$ ,  $\hat{D}$ ?

(b) For  $\text{Cap} = 1F$ ,  $L = 1H$  and  $R = 1\Omega$ , compute the matrix exponential  $e^{\hat{A}t}$ . Hence for  $u = \mathbb{I}$ , compute the states  $x_1$ ,  $x_2$ , and the output  $y$ . Identify the transient and steady state parts of each one of these functions.

(c) Compute the transfer function of this system; from this, or otherwise, deduce the differential equation relating  $y$  and  $u$ , and compute the impulse response. ■